
Technician Question Pool

July 2022 to June 2026

The MORE Project

<http://n2re.org/m-o-r-e-project>



Electrical Principles

No-Nonsense pages 11 - 13

Ohm's Law

Hams obey Ohm's Law! $E = I \times R$

Ohm's Law is the relationship between voltage, current, and resistance in an electrical circuit.

When you know any two of these values, you can calculate the third.



T5D02

What formula is used to calculate voltage in a circuit?

- A. $E = I \times R$
- B. $E = I / R$
- C. $E = I + R$
- D. $E = I - R$



EP2 Q1 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D02

What formula is used to calculate voltage in a circuit?

A. $E = I \times R$

B. $E = I / R$

C. $E = I + R$

D. $E = I - R$



T5D03

What formula is used to calculate resistance in a circuit?

A. $R = E \times I$

B. $R = E / I$

C. $R = E + I$

D. $R = E - I$



T5D03

What formula is used to calculate resistance in a circuit?

A. $R = E \times I$

B. $R = E / I$

C. $R = E + I$

D. $R = E - I$



T5D01

What formula is used to calculate current in a circuit?

- A. $I = E \times R$
- B. $I = E / R$
- C. $I = E + R$
- D. $I = E - R$



EP2 Q3 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D01

What formula is used to calculate current in a circuit?

A. $I = E \times R$

B. $I = E / R$

C. $I = E + R$

D. $I = E - R$



T5D04

What is the resistance of a circuit in which a current of 3 amperes flows when connected to 90 volts?

- A. 3 ohms
- B. 30 ohms
- C. 93 ohms
- D. 270 ohms



EP2 Q4 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D04

What is the resistance of a circuit in which a current of 3 amperes flows when connected to 90 volts?

- A. 3 ohms
- B. 30 ohms**
- C. 93 ohms
- D. 270 ohms



T5D05

What is the resistance in a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?

- A. 18 ohms
- B. 0.125 ohms
- C. 8 ohms
- D. 13.5 ohms



T5D05

What is the resistance in a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?

- A. 18 ohms
- B. 0.125 ohms
- C. 8 ohms**
- D. 13.5 ohms



T5D06

What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

- A. 3 ohms
- B. 16 ohms
- C. 48 ohms
- D. 8 ohms



T5D06

What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

- A. 3 ohms
- B. 16 ohms
- C. 48 ohms
- D. 8 ohms



T5D07

What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

- A. 9600 amperes
- B. 200 amperes
- C. 0.667 amperes
- D. 1.5 amperes



T5D07

What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

- A. 9600 amperes
- B. 200 amperes
- C. 0.667 amperes
- D. 1.5 amperes**



T5D08

What is the current through a 100-ohm resistor connected across 200 volts?

- A. 20,000 amperes
- B. 0.5 amperes
- C. 2 amperes
- D. 100 amperes



EP2 Q8 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D08

What is the current through a 100-ohm resistor connected across 200 volts?

- A. 20,000 amperes
- B. 0.5 amperes
- C. 2 amperes**
- D. 100 amperes



T5D09

What is the current through a 24-ohm resistor connected across 240 volts?

- A. 24,000 amperes
- B. 0.1 amperes
- C. 10 amperes
- D. 216 amperes



T5D09

What is the current through a 24-ohm resistor connected across 240 volts?

- A. 24,000 amperes
- B. 0.1 amperes
- C. 10 amperes**
- D. 216 amperes



T5D10

What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

- A. 1 volt
- B. 0.25 volts
- C. 2.5 volts
- D. 1.5 volts



EP2 Q10 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D10

What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

- A. 1 volt
- B. 0.25 volts
- C. 2.5 volts
- D. 1.5 volts



T5D11

What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?

- A. 1 volt
- B. 10 volts
- C. 11 volts
- D. 9 volts



EP2 Q11 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D11

What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?

- A. 1 volt
- B. 10 volts**
- C. 11 volts
- D. 9 volts



T5D12

What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?

- A. 8 volts
- B. 0.2 volts
- C. 12 volts
- D. 20 volts



EP2 Q12 of 12

FCC Tech 7/22 to 6/26
Ohm's Law

n2re.org/m-o-r-e-project

T5D12

What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?

- A. 8 volts
- B. 0.2 volts
- C. 12 volts
- D. 20 volts**





A non-profit initiative by the IEEE and ARDC to increase the numbers of youth (12-18) and non-males in Amateur Radio. Participants earn FCC licenses and receive free 2-way radios.

For MORE information: n2re.org/m-o-r-e-project
Dr. Rebecca Mercuri, Grant Administrator, rtmercuri@ieee.org



n2re.org/m-o-r-e-project