# Technician Question Pool July 2022 to June 2026

#### **The MORE Project**


http://n2re.org/m-o-r-e-project




## Electrical Principles No-Nonsense pages 14 - 15


#### **Series & Parallel Circuits**

Resistors in series:

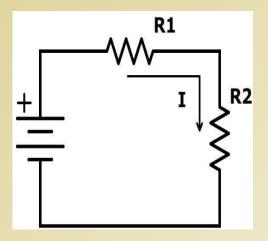


Resistors in parallel:

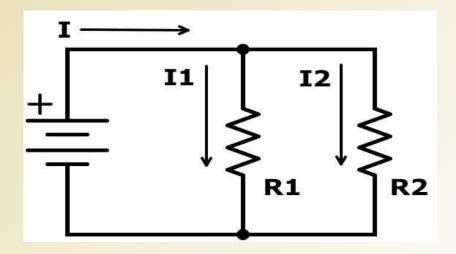

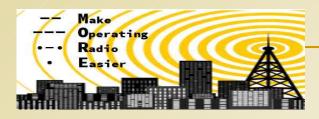

In which type of circuit is DC current the same through all components?

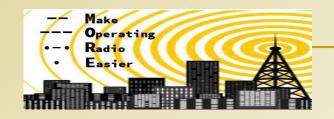- A. Series
- B. Parallel
- C. Resonant
- D. Branch




In which type of circuit is DC current the same through all components?

- A. Series
- B. Parallel
- C. Resonant
- D. Branch



In which type of circuit is voltage the same across all components?

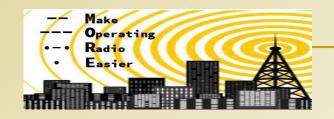- A. Series
- B. Parallel
- C. Resonant
- D. Branch



In which type of circuit is voltage the same across all components?

- A. Series
- **B.** Parallel
- C. Resonant
- D. Branch





A non-profit initiative by the IEEE and ARDC to increase the numbers of youth (12-18) and non-males in Amateur Radio. Participants earn FCC licenses and receive free 2-way radios.

For MORE information: n2re.org/m-o-r-e-project Dr. Rebecca Mercuri, Grant Administrator, rtmercuri@ieee.org

