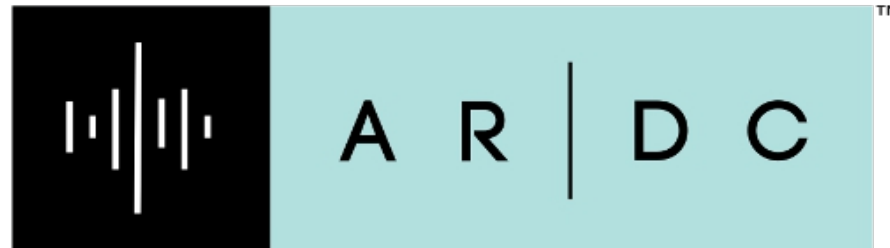


# Amateur Radio Technician Class Training

Slideset created by Alan Wolke, W2AEW  
Permission granted for use by the MORE Project

Based on the No-Nonsense Technician Class  
Study Guide by Dan Romanchik, KB6NU

Updates by Rebecca Mercuri, Ph.D., K3RPM



AMATEUR RADIO DIGITAL COMMUNICATIONS




**Welcome to Session 2**

**Any Questions Before We Start?**
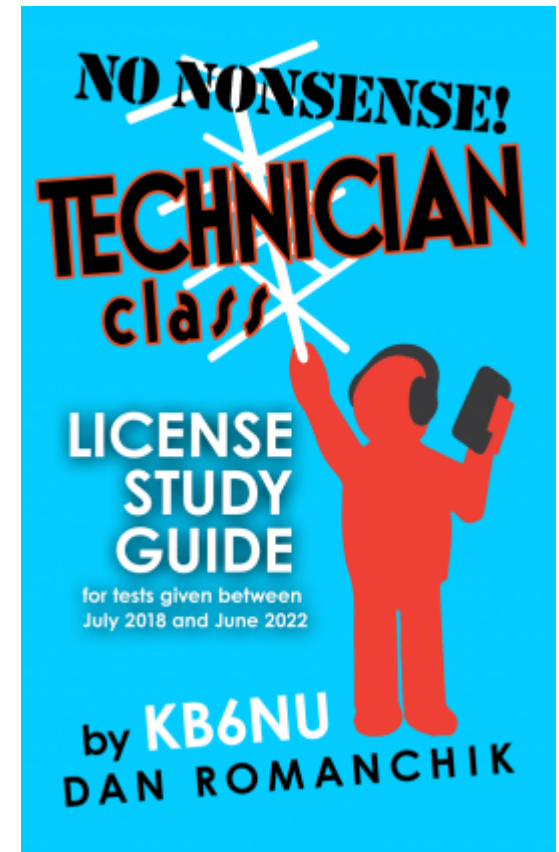
# Agenda



- Introduction
- Radio Wave Characteristics (RWC)
- **Electronic Components and Circuits (ECCD)**
- **Electrical Principles (EP)**
- Antennas and Feed Lines (AFL)
- Amateur Radio Signals (ARS)
- Electrical Safety (ES)
- Radio Practices and Station Setup (RPSS)
- Station Equipment (SE)
- Operating Procedures (OP)
- Rules and Regulations (RR)




# Electronic Components & Circuit Diagrams (ECCD)

- Resistors, Capacitors, ...
- Semiconductors
- Circuit Diagrams
- Other Components
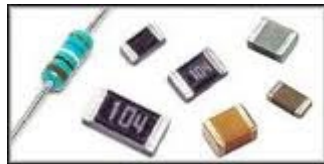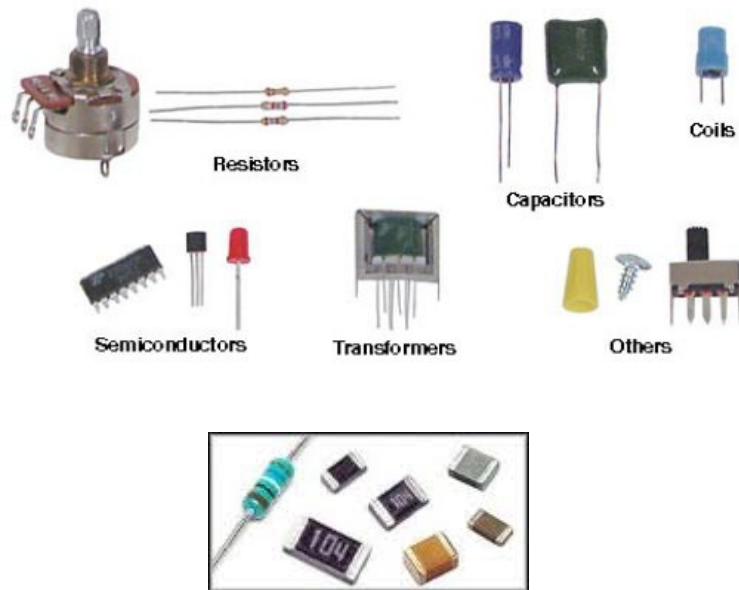
# Electronic Components & Circuit Diagrams (ECCD)




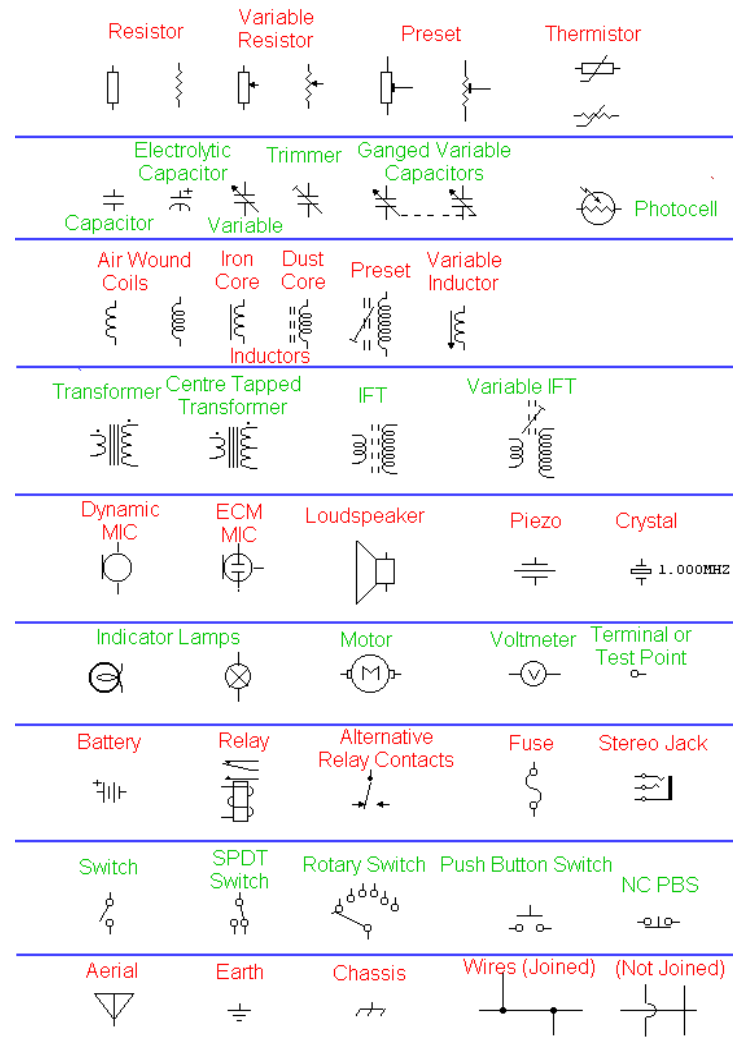
***These are just examples -- only need to memorize the circuits and components on slides 16, 17, 18 in this set***


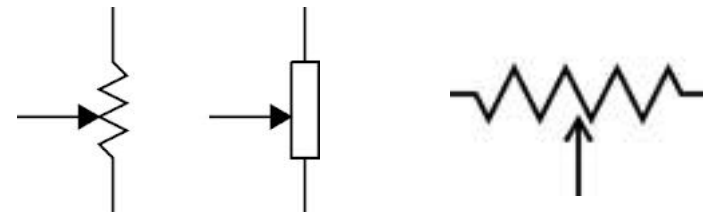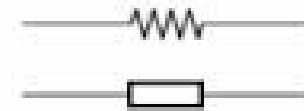
# Resistors

Passive Components



- **Resistors** oppose the flow of current
- Variable resistors are called **Potentiometers** (or **Rheostats**)
- Resistor value expressed in **ohms**



# Capacitors
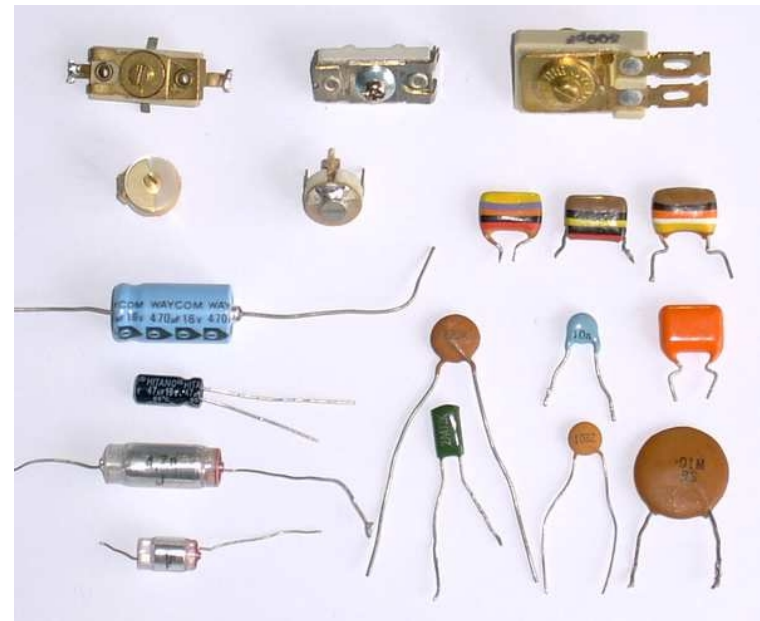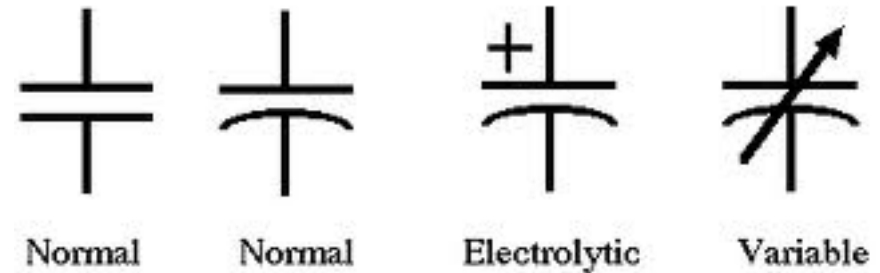
## Passive Components


- Two conductors separated by an insulator (or dielectric) is a **Capacitor**
- Stores energy in an *electric* field
- Capacitance is the ability to store energy in an electric field
- The unit of measure is the **Farad**


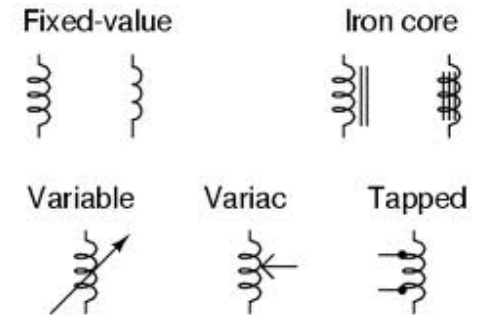
# Inductors

Passive Components

- An **inductor** stores energy in a *magnetic* field
- Often just a coil of wire!
- The ability to store energy in a magnetic field is called **Inductance**
- Unit of measure is **Henry**






# Switches
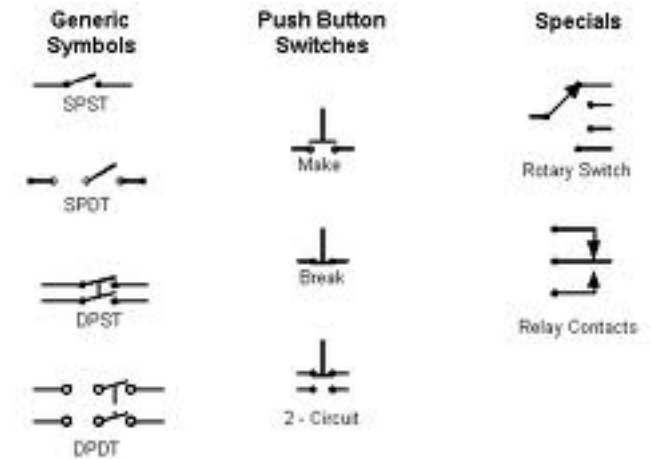
## Passive Components

- Used to connect and disconnect electrical circuits
- **Pole:** “movable part”
- **Throw:** where the pole can get moved to
- SPST: single-pole, single-throw
- DPDT: double-pole, double-throw



# Fuses

## Passive Components

- Protects circuits from overload (excessive current)
- “Blown” fuse – breaks and has to be replaced, but circuit should be checked first to see what caused the overload
- Rated in **Amps**



# Batteries

**Primary** batteries are not rechargeable:


Carbon Zinc, Alkaline

**Secondary** batteries are rechargeable:

NiCad, NiMH, Lithium-ion, LiFePO4

Different types have different voltages

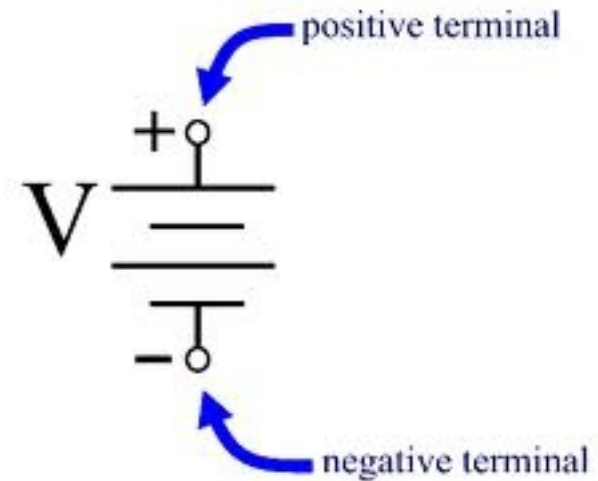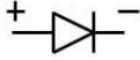

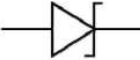

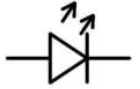

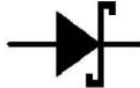

NiCad typically 1.2V



# Diodes

## Semiconductors


- Allows current to flow in only one direction
- Terminals are:
  - Anode (+)*
  - Cathode (-)*
- Cathode has the *stripe*
- Often called **Rectifier**

Name	Symbol	Image
Diode		
Zener Diode		
LED (Light Emitting Diode)		
Schottky Diode		
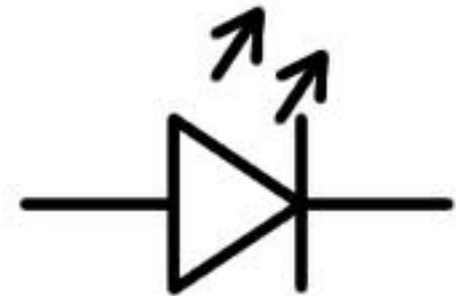
# Light Emitting Diodes (LEDs)

Semiconductors

- A diode that creates light when current passes through it
- Commonly used as a *visual indicator*



# Transistors

## Semiconductors

- Component where *current* flow is controlled by another *current or voltage*
- Used as a *switch* or *amplifier*
- **Gain** is a measure of the ability to amplify
- Ratio of output to input current (for example)



# Some Transistor Types

- **Bipolar transistors** are made of *three layers* of semiconductor



NPN or PNP

- **Terminals are:**

Base

Collector

Emitter

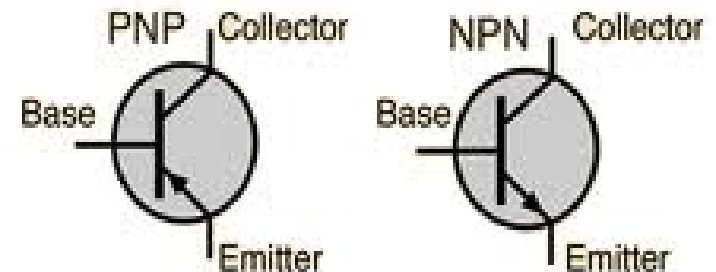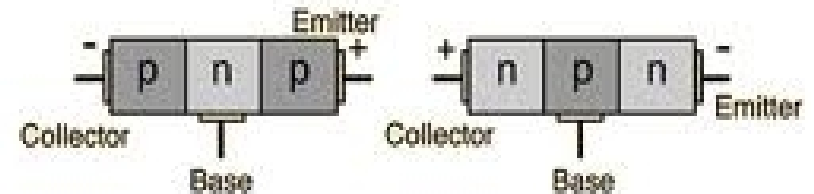

# More Transistor Types


## Field Effect Transistor (FET)

- Current is controlled by voltage on the Gate
- Terminals are:

Gate

Drain

Source

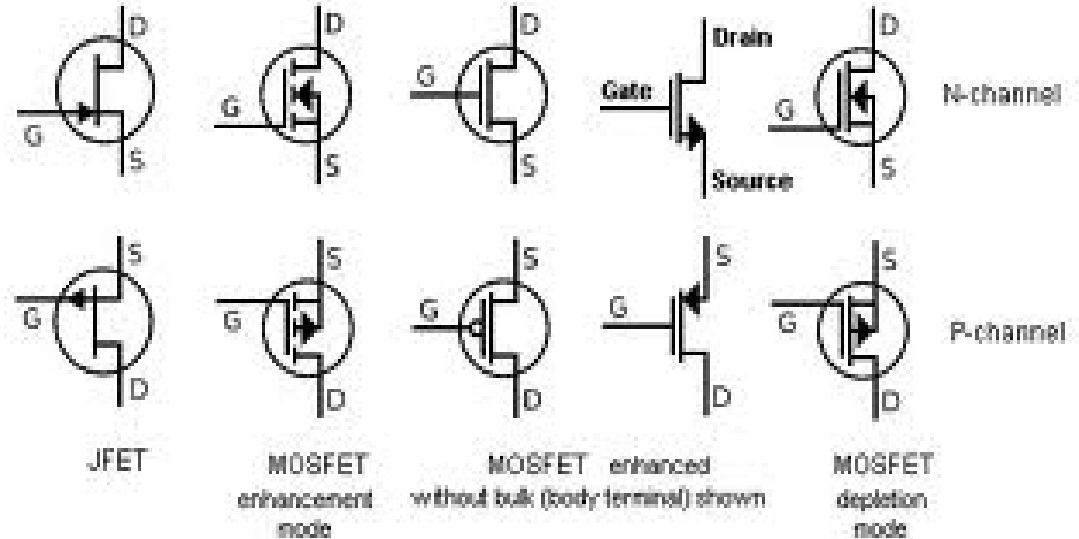




# Schematic Symbols

Examples of Circuit Diagrams  
(do not memorize this page)
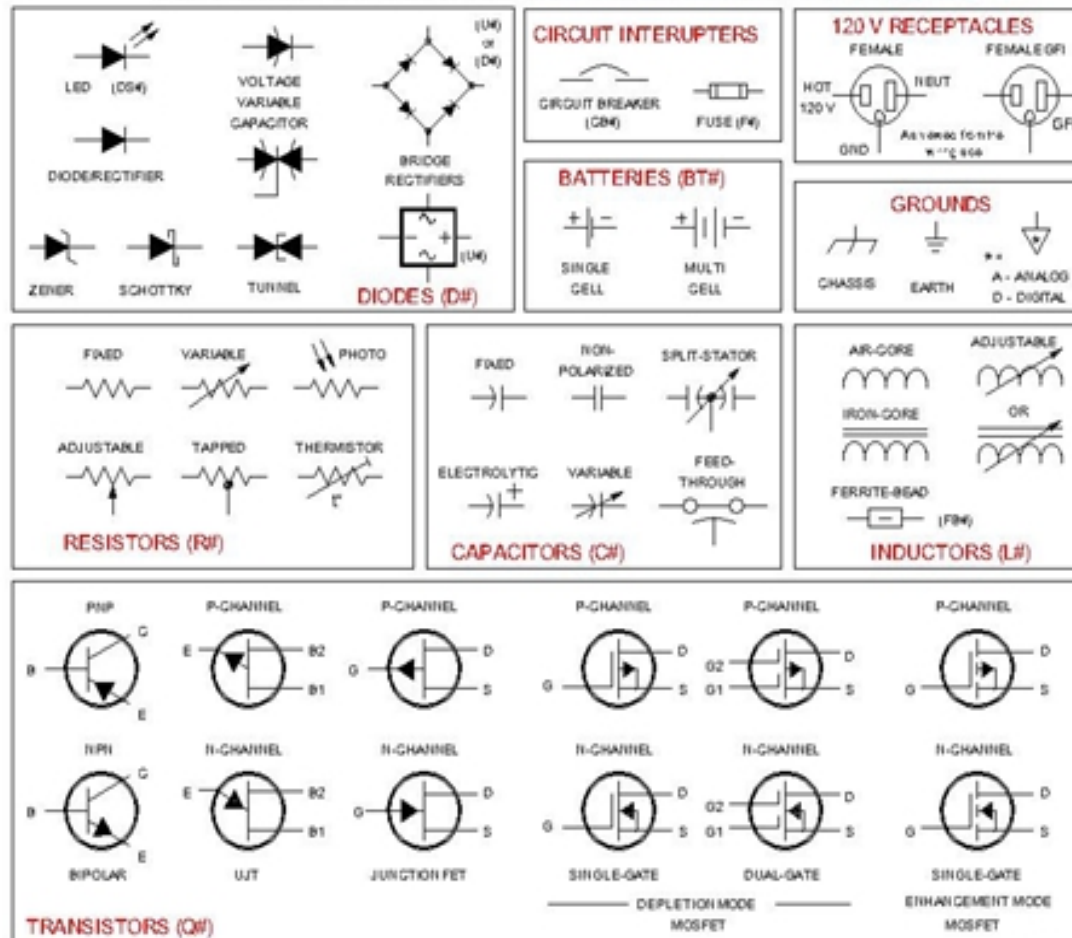
## Schematic Symbols Used in Circuit Diagrams

Labeling conventions: # is a sequential number. (X#) is the component designator. Examples - C3, L11, R8, Q3





© 1994 by HOOPER

# Schematic Symbols

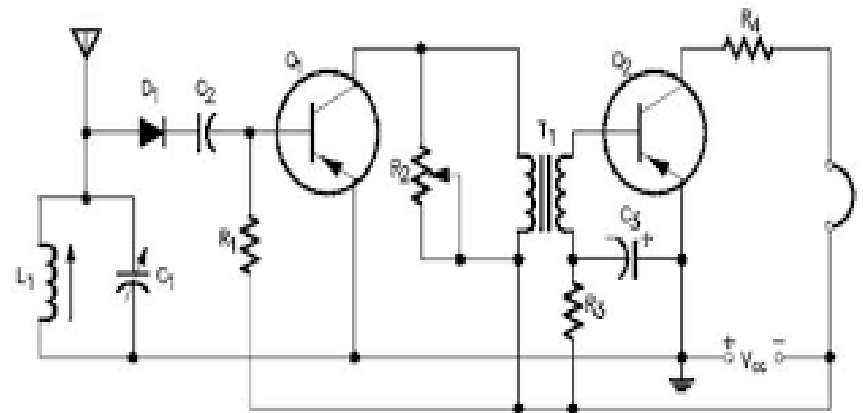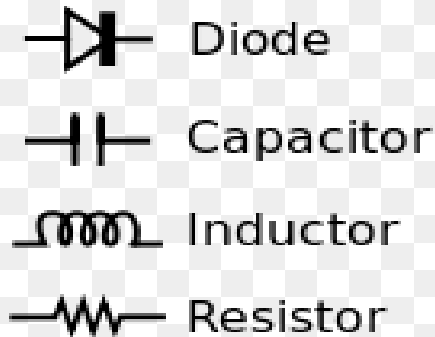
## Circuit Diagrams

- Schematic **symbols** are standardized representations for *components*
- Schematic **diagram** depicts the *interconnections* between components that make up a circuit



# Schematic Diagrams


## Circuit Diagrams

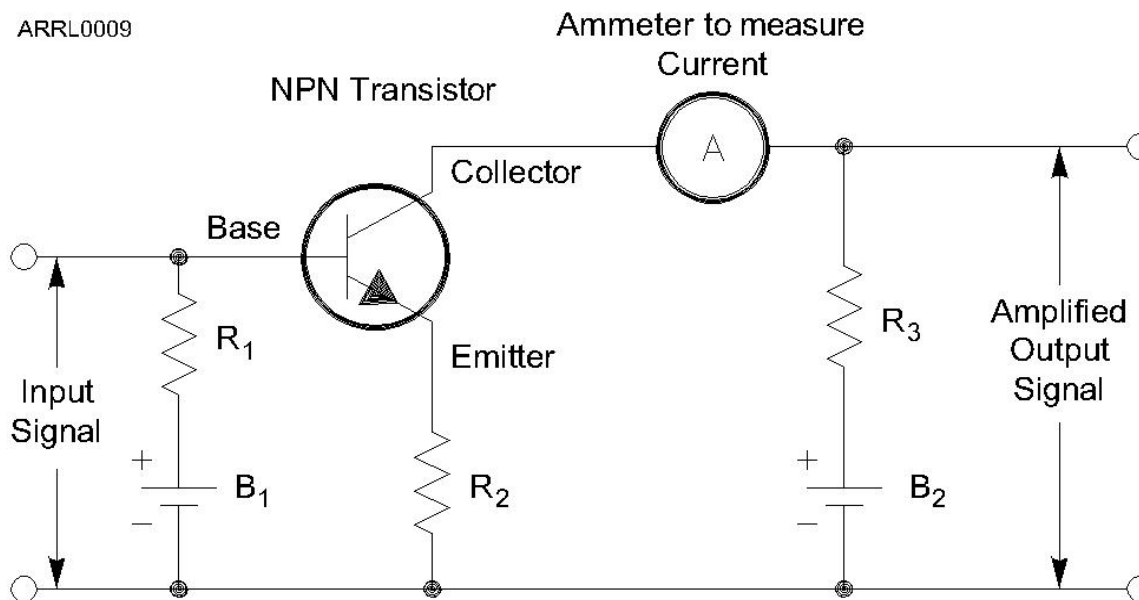

# Schematic Diagram Examples

## Circuit Diagrams – Need to Memorize

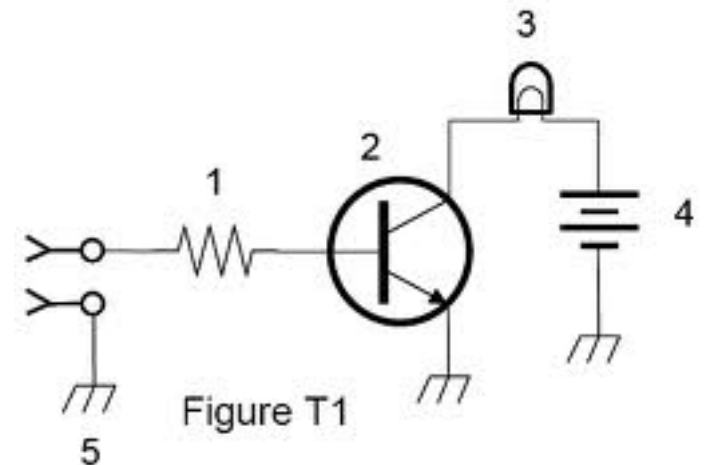- 1: **Resistor**, used to limit input current
- 2: **Transistor**, controls the flow of current through the lamp
- 3: **Lamp**
- 4: **Battery**, supplies current to light the lamp
- 5: **Ground** to chassis



Turns on a light when a positive voltage is applied to the input

# Schematic Diagram Examples

## Circuit Diagrams – Need to Memorize

1: **Power Connector**

2: **Fuse**

3: **Single Pole, Single Throw switch (SPST)** to turn the power supply on/off

4: **Transformer**, used to change 120VAC to lower AC voltage

5: **Rectifier diode** to change AC to a varying DC signal

6: **Capacitor** helps to remove the 60Hz variation in the signal (filter)

7: **Resistor**

8: **LED** – pilot light to show it is on

9: **Variable Resistor** to vary the output current

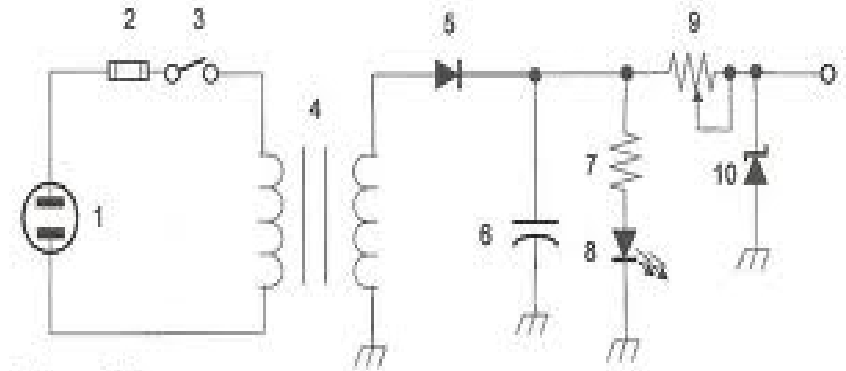


Figure T2

## Simple AC – DC Power Supply

# Schematic Diagram Examples

Circuit Diagrams – Need to Memorize

2: **Variable Capacitor**

3: **Variable Inductor**

The variable capacitors together with the variable inductor together create a *tuned circuit*

*Capacitors and inductors connected together are often filters or tuned/resonant circuits*

4: **Antenna**

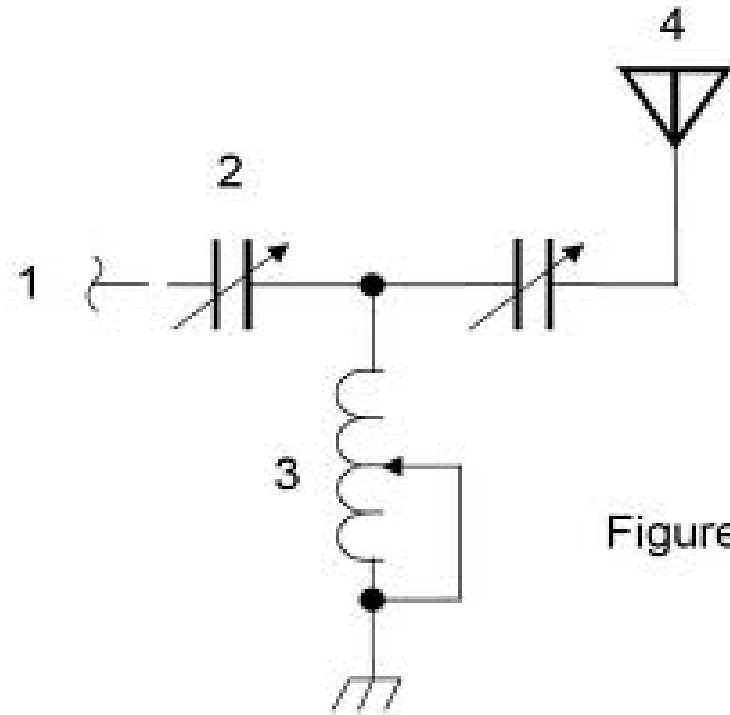


Figure T3

Output circuit of a transmitter

# Other Components

## Circuit Diagrams

**Relay:** a switch controlled by an electromagnet

**Meter:** used to display a electrical quantity on a numeric scale

**Shielded Wire:** prevents coupling of unwanted signals to/from the wire

**Regulator:** controls the amount of voltage from a power supply

**Integrated Circuit:** combines many parts in one package, performs analog and/or digital functions

# Electronic Components & Circuit Diagrams Chapter End

Questions?

Let's Practice for the Exam!




# Electrical Principles (EP)

- Units and Terms
- Ohm's Law
- Series & Parallel
- DC Power
- Math
- Decibels


# Why Do We Start With Electrical Principles?

- While Hams can operate amateur radios “out of the box” without modifications, it is important to know the underlying electrical fundamentals
- Designing, building and repairing amateur radio components is also an interest of many Hams
- This knowledge is required by the FCC -- the formulas we provide here will help you answer the exam questions on these topics
- This information is covered first in the MORE Course so that you will have the longest amount of time to review and remember it

# Electrical Principles (EP)

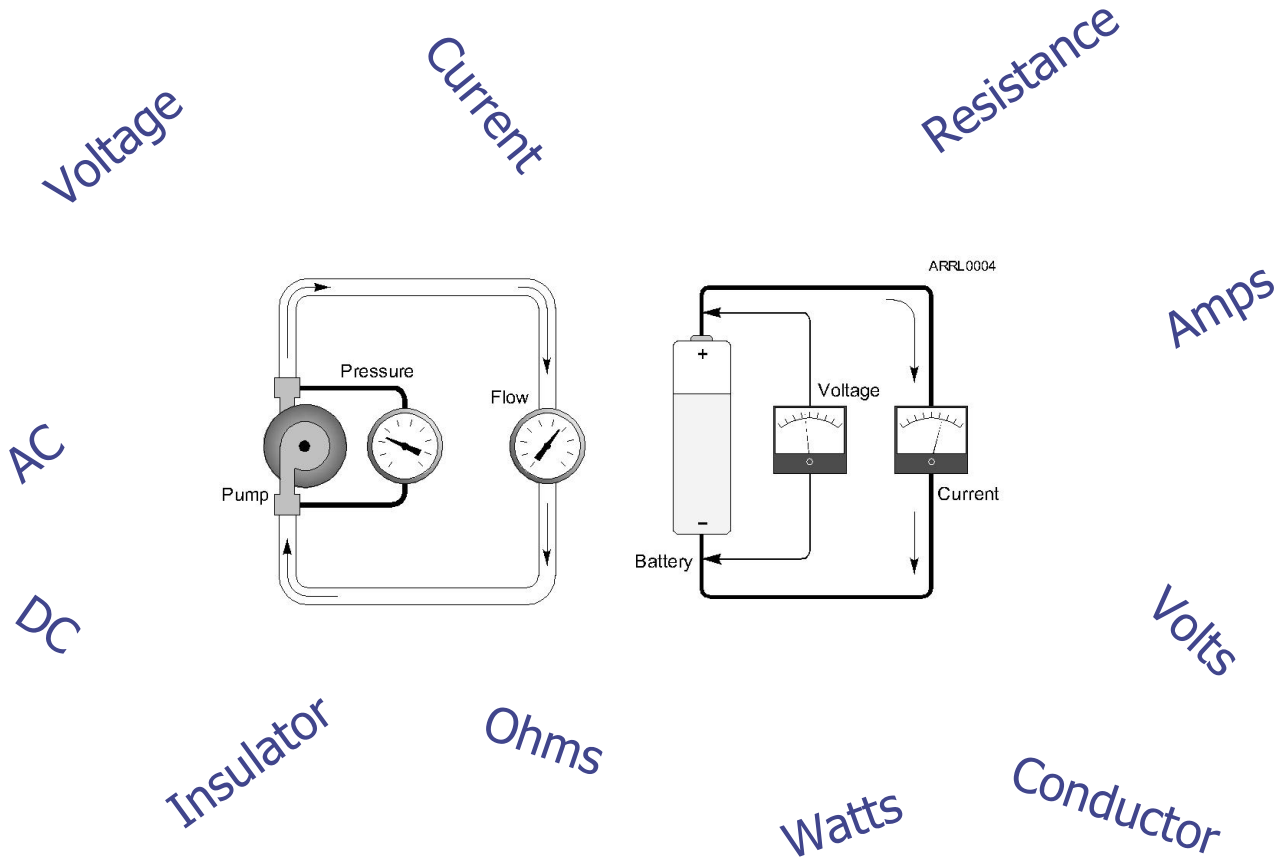


# Voltage

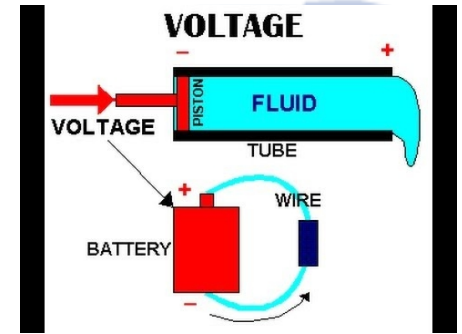

- The **force** that pushes electrons around
- Also called Electro-Motive Force: **EMF**
- Measured in units called **VOLTS**
- Measured with a **Voltmeter**
- Symbol is **E**, unit symbol is **V**
- Typical mobile radios require 12 volts to operate

# Current


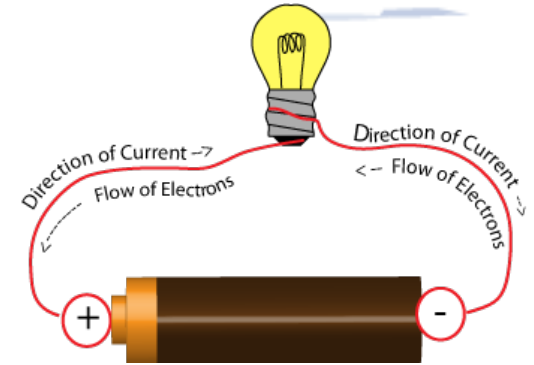


- The *flow of electrons* in a circuit
- Measured in units of **Amperes** (amps)
- Symbol is **I**, units symbol is **A**
- Measured with an **Ammeter**
- **DC**: Direct Current flows in one direction
- **AC**: Alternating Current flows back and forth, *changing direction on a regular basis*


# AC = Alternating Current

**Frequency:** number of times per second that an alternating current makes a complete cycle

**Hertz:** Unit of frequency

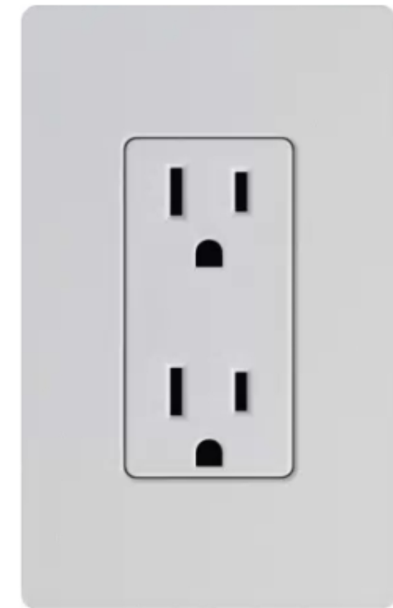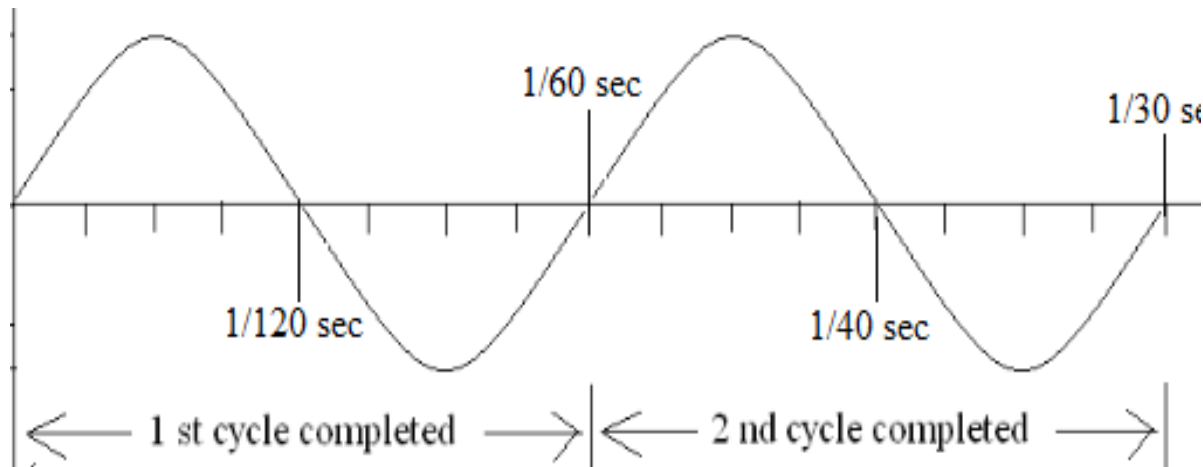


# Resistance

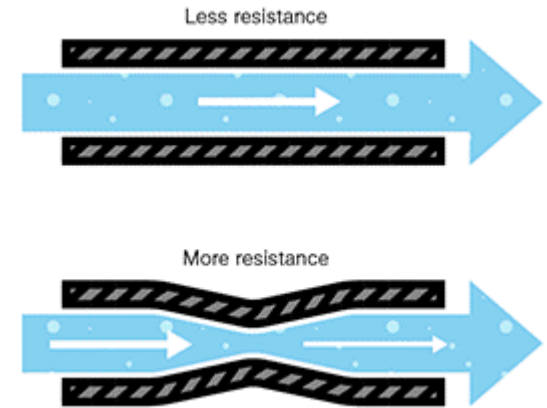

- Opposes the flow of electrons
  - Higher resistance -> smaller current
- Measured in ***Ohms***
- Symbol is ***R*** Unit symbol is  **$\Omega$**
- Measured with an ***Ohmmeter***

# Conductors & Insulators

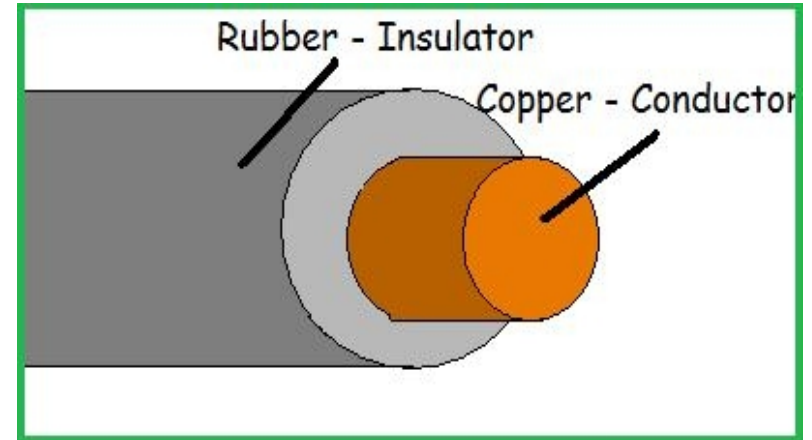

- **Conductors**

- Low resistance, allow current to flow
- Copper, aluminum, gold, silver, etc.

- **Insulators**

- High resistance, little/no current flow
- Plastic, wood, glass, mica, paper, etc.



# Power



- *Rate* at which electrical energy is used
- Measured in **Watts**
- Symbol is **P** Unit symbol is **W**
- Often not measured directly, but calculated –  
*more on this shortly...*

# Summary of Terms


- EMF (E) is measured in Volts (V)
- Current (I) is measured in Amps (A)
- Resistance (R) is measured in Ohms ( $\Omega$ )
- Power (P) is measured in Watts (W)

***Memorize this!***

# Ohm's Law

Relationship between:

- Voltage
- Current
- Resistance

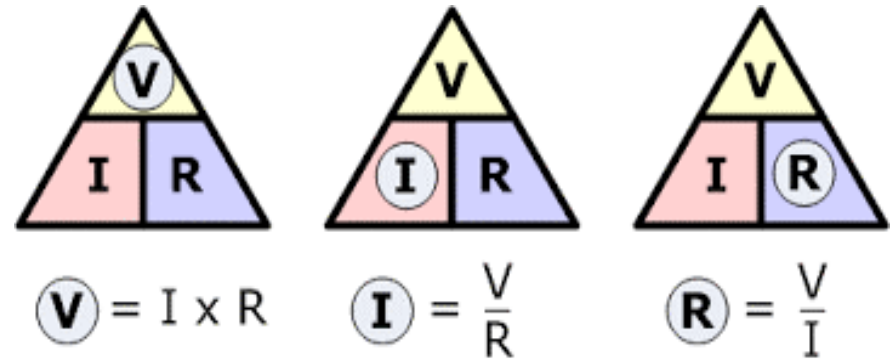


Voltage = Current x Resistance

$$E = I \times R$$

$$I = E / R$$

$$R = E / I$$

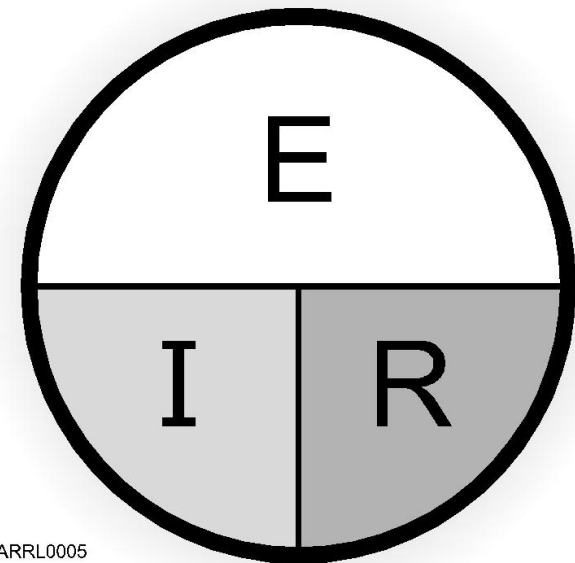

# Ohm's Law Calculations

USING THE "MAGIC" FORMULA CIRCLE TO DO MATH.

TOP TO BOTTOM DIVIDE.

SUCH AS:

$$12 \div 8 = 1.5$$


$$12 \div 1.5 = 8$$

SIDE TO SIDE MULTIPLY.


SUCH AS:

$$8 \times 1.5 = 12$$

$$1.5 \times 8 = 12$$

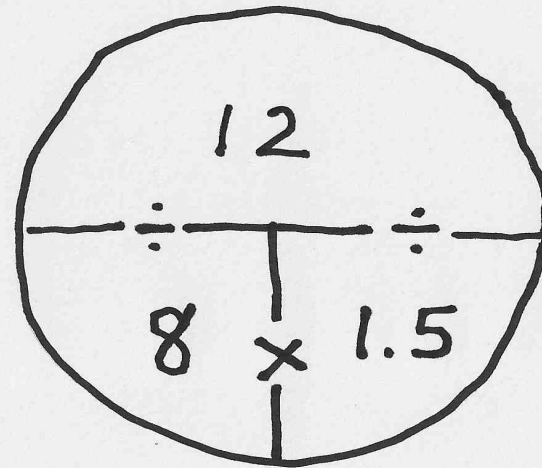

# Ohm's Law Examples

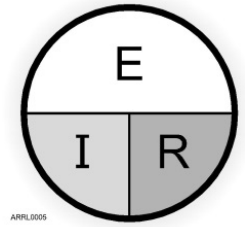

- 90 volts is applied across a resistor resulting in 3 amperes of current. What's the resistance?

$$R = E / I \quad 90V/3A = \mathbf{30\Omega}$$

- 12 volts applied to a circuit with 8 ohms of resistance – how much current flows?


$$I = E / R \quad 12V/8\Omega = \mathbf{1.5 \text{ amperes}}$$

- 2A flowing through 10Ω resistor – what voltage appears across the resistor?


$$E = I \times R \quad 2A \times 10 \Omega = \mathbf{20 \text{ Volts}}$$

# Series and Parallel Circuits


- **Series:** devices are end-to-end

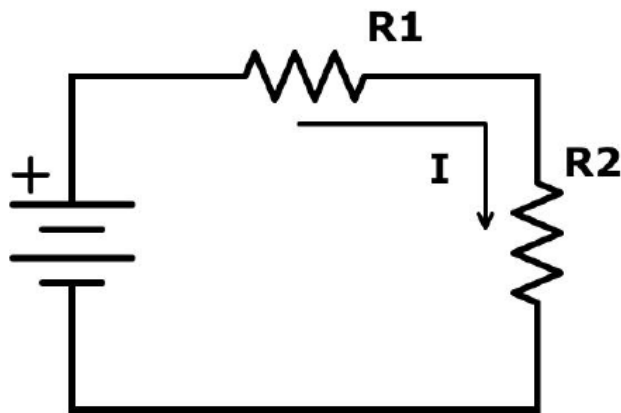

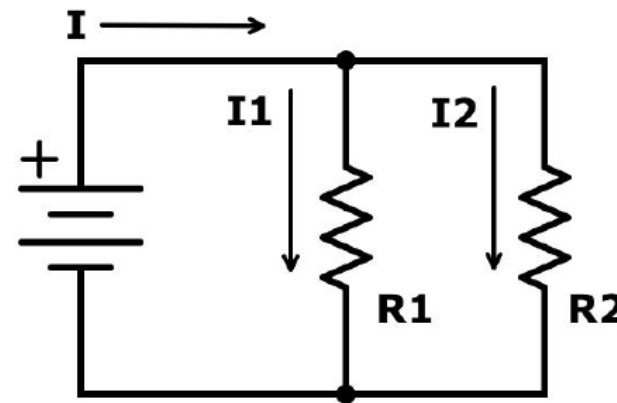- **Parallel:** devices are next to each other




# Series Circuits

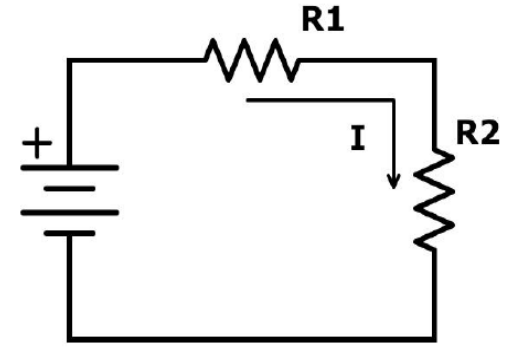

- There is *one path* for current to flow
- **Current** is:
  - the *same through all components*
  - is *unchanged* at component junctions
- **Voltage** across each component is *determined by type and value* of each component.
- Sum of voltages across components equals the voltage source

# Parallel Circuits

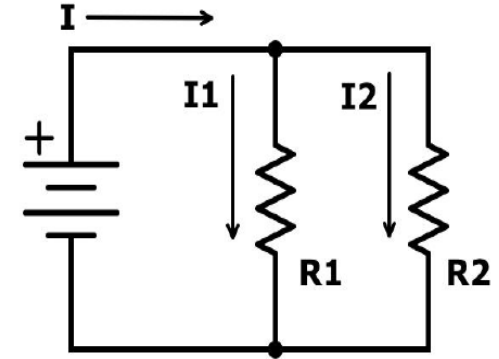

- Each component connected to voltage source (in this example)
- **Voltage** across each component is the *same*
- **Current** divides at component junctions, *dependent on component values*
- Sum of currents in each component equals total current from the source



# Calculating Power

Relationship between:



- Power
- Voltage
- Current

Power is Voltage x Current

$$P = E \times I$$

$$E = P / I$$

$$I = P / E$$

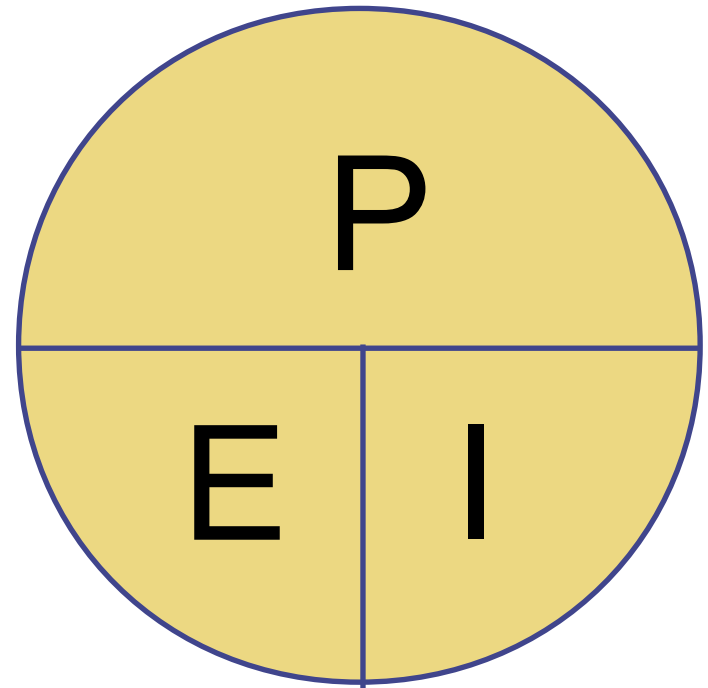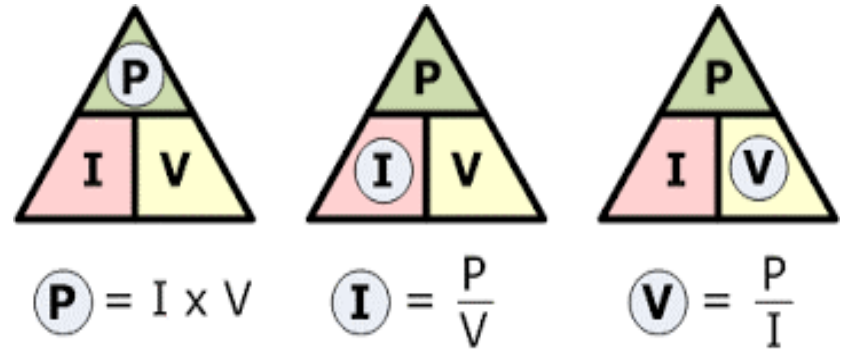

# Power Law Calculations

USING THE "MAGIC" FORMULA CIRCLE TO DO MATH.

TOP TO BOTTOM DIVIDE.

SUCH AS :


$$138 \div 10 = 13.8$$

$$138 \div 13.8 = 10$$


SIDE TO SIDE MULTIPLY.

$$13.8 \times 10 = 138$$

$$10 \times 13.8 = 138$$

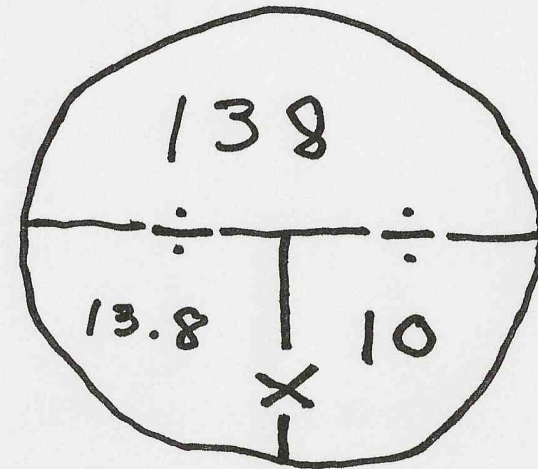

# Power Examples

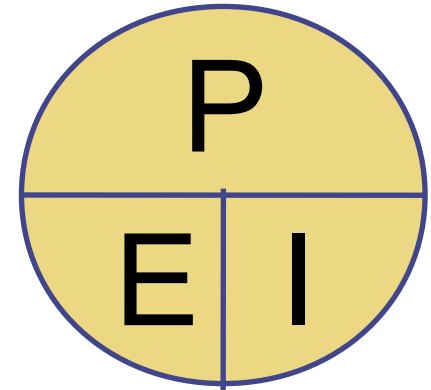

- How much power is being used by a circuit that draws 10A from a 13.8V source?

$$P = E \times I \quad 13.8V * 10A = \mathbf{138 \text{ Watts}}$$

- Applied voltage is 12V and current is 2.5A, what is the power?

$$P = E \times I \quad 12V \times 2.5A = \mathbf{30W}$$

- With 12V applied and 120W used, what is the current?

$$I = P / E \quad 120W / 12V = \mathbf{10 \text{ A}}$$

# Math for Electronics: Prefixes

Used with electrical quantities

**milli** = 1/1000th, such as **1mA** is 1/1000th of an ampere, or 0.001A

**micro** = 1/1,000,000th (one millionth), such as **3μV** which is 0.000003V

**pico** = 1 trillionth (millionth of a millionth)  
such as **5pA** = 0.000005μA

# Prefixes continued

**kilo** = 1000x, such as **1kV** = 1000V

**mega** = 1 million times (1,000,000x)  
such as **1MΩ** = 1,000,000Ω

**giga** = 1 billion times, such as **2.4GHz**

Prefixes are often used on many different electrical quantities

# Prefix Examples

- 1,500 milliamperes = 1.5 amperes
- 1,000 volts = 1 kilovolt (1kV)
- 1 millionth of a volt = 1 microvolt (1 $\mu$ V)
- 3000mA = 3A
- 3500 kilohertz = 3.5 megahertz (**MHz**)
- 2425 MHz = 2.425 GHz

# Decibels (dB)

- When dealing with loudness and power ratios we use decibels
- Easy to express large ratios with small numbers
- Decibels use a logarithmic (log) scale
- Cascading ratios multiply or divide but cascading decibels add or subtract
- +dB represents an "increase"  
- dB represents a "decrease"

# Decibel Ratios to Remember

- **3dB** is a factor of **2x**

A change from 5W to 10W is a 3dB increase, a ratio of 2 to 1

- **6dB** is a factor of **4x**

A change from 12W to 3W is a 6dB decrease (-6dB change), ratio of 4 to 1

- **10dB** is a factor of **10x**

20W to 200W is a 10dB increase, ratio of 10 to 1

- Combinations (dB values add and subtract)

13dB change is a factor of 20x (10 x 2)



# Electrical Principles

## Chapter End

Questions?

Let's Practice for the Exam!